

HW1: Boolean Algebra

1. **Drawing Boolean Equations as Circuits:** Draw out the following logic equations without simplifying them first, using 1, 2, or 3-input logic gates.

a. $X = \overline{(AB + CD)}$

b. $Y = A\overline{(B + \overline{CD})}$

c. $Z = \overline{(A + B)} \cdot \overline{(C + \overline{D})}$

2. **Simplifying Boolean Expressions:** Simplify the following expressions using algebraic manipulation (show steps):


a. $w + (w\bar{x}yz)$

b. $xz + \bar{x}y + zy$ Hint: Consensus Theorem $AB + A'C + BC = AB + A'C$


c. $x[x + (xy)]$

d. $(A + C)(\bar{A} + B)(B + C)$

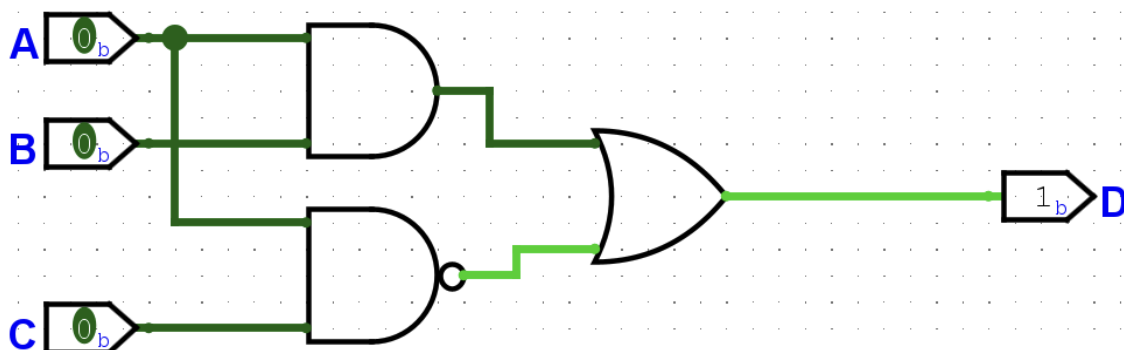3. Find the equation of the following circuits (do not optimize):



(i) $D(A,B,C) =$

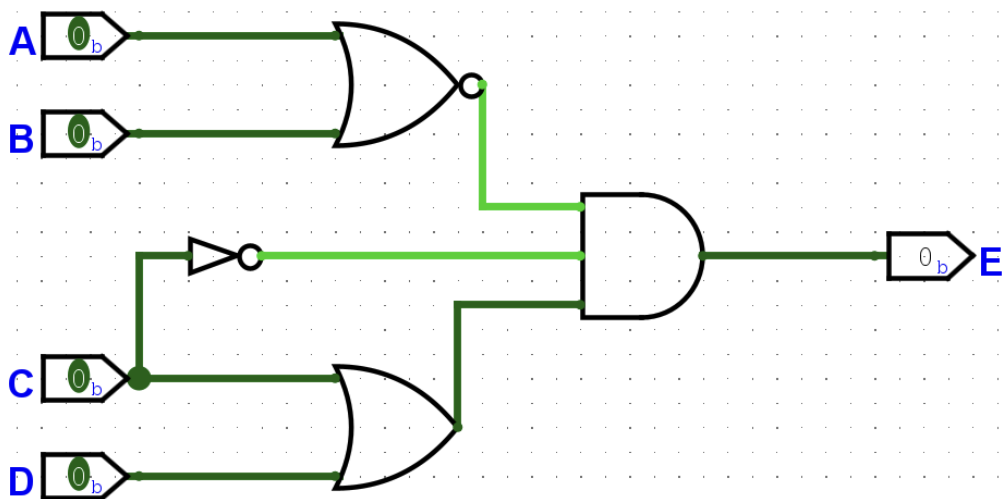

(ii) $E(A,B,C, D) =$