

# Digital Logic And Computing Systems

Lecture 06 – Automata – Controlpath - Cont

Dr. Christophe Bobda  
EEL3701C Fall 2025

# Agenda

- Introduction and Motivation
- Sequential Circuits
- Mealy- and Moore Automata
- Design of Sequential Circuits
- Case studies

# Controllers Design

- So far, we have discussed combinational circuits
- Ex. Coffee dispenser
  - Select a coffee type (espresso, cappuccino, regular, etc...) → 3 buttons
  - Select size (small, medium, large) → 3 buttons
  - Select sugar option → 1 – 2 buttons
  - Select milk option → 1-2 buttons
  - Pay (cash or card) → ?? 4 – 6?
- A combinational circuit would require
  - All inputs at once → **not usable**
  - Too many buttons for all possible options → **too expensive**
- **Solution: Sequential Circuits**
  - Multipurpose inputs → **less expensive**
  - One-at-a-time entry → **convenient, user friendly**



# Sequential Circuits - Modeling with Automata


- Design a controller for a vending machine that can deliver

- 15-Ct candy
- 20-Ct candy

- The vending machine accepts

- 5 ct
- 10 ct

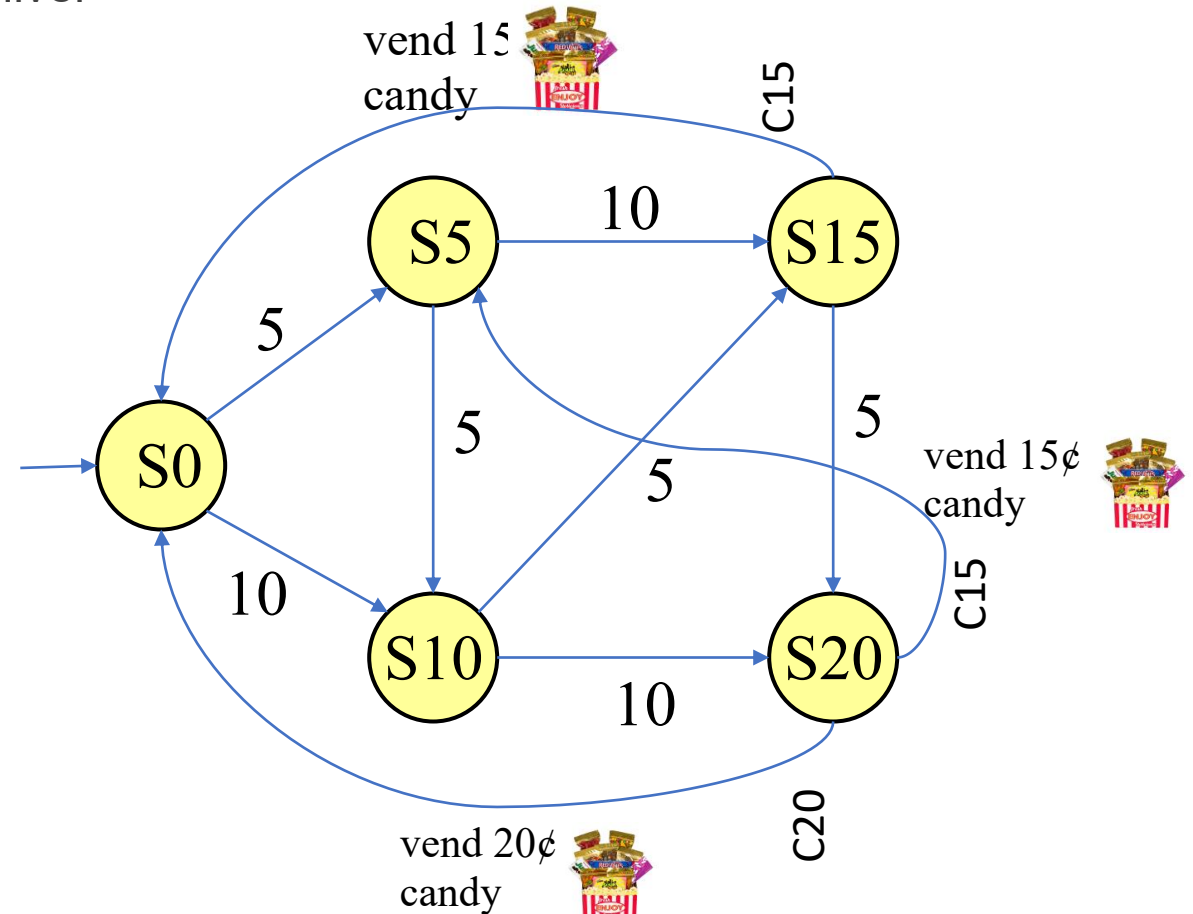- And delivers the 15-ct or 20-ct candy, based on the user's choice



# Sequential Circuits

- Outputs in combinational circuits are functions of the inputs only.
  - Circuits with high number of inputs require **large input “alphabet”**.
    - Technologically difficult and expensive to realize.
    - Impossible to use.
  - A **sequential circuit** is a circuit whose outputs depend on the **current** and **previous** inputs.
    - Memory is required to store the circuit's **state**.
  - We need a viable model, **to describe, analyze, optimize and implement a sequence of actions**.

→ Finite State Automata (Finite State Machine).

# Mealy-Automata

Definition: A **Mealy-Automaton** is a tuple  $A=(X, Y, S, \delta, \lambda, s_i)$ , where

$X$ : finite, non-empty set of **input symbols**

$Y$ : finite, non-empty set of **output symbols**

$S$ : finite, non-empty set of **states**


$\delta: S \times X \rightarrow S$       **State transition function**

$\lambda: S \times X \rightarrow Y$       **Output function**

$s_i$ :                      **Initial state**


**State set finite**  $\rightarrow$  finite state automata (finite state machine, FSM)

 - Mealy-Automata can uniquely be represented through
  - a state transition table or
  - state transition diagram (graph)


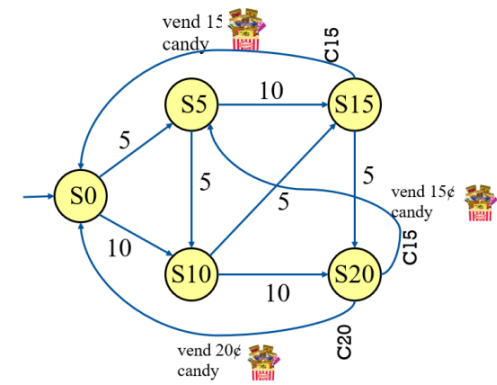
# Mealy – State Transition Table

- A state transition table is a table in which the rows represent states and columns represent input symbols.
  - An entry  $(\delta(s,x) / \lambda(s,x))$  captures the transition from state  $s \in S$  with input symbol  $x \in X$  to state  $\delta(s,x)$  with output  $\lambda(s,x)$
- Example




$$X = \{x_1, x_2, x_3\}, \quad Y = \{y_1, y_2\}, \quad S = \{s_1, s_2, s_3, s_4\}, \quad s_I = s_1$$


$\delta / \lambda$	$x_1$	$x_2$	$x_3$
$s_I = s_1$	$s_2 / y_1$	$s_3 / y_2$	$s_2 / y_1$
$s_2$	$s_1 / y_2$	$s_3 / y_2$	$s_2 / y_1$
$s_3$	$s_3 / y_1$	$s_2 / y_1$	$s_4 / y_1$
$s_4$	$s_3 / y_2$	$s_1 / y_2$	$s_4 / y_2$
 
# Mealy – State Transition Graph

- A state transition graph is a directed graph in which nodes represent states, and edges represent transitions
  - Edges are labeled with the values of the transition function
  - The node without precedence represents the initial state




## ■ Example

 

$$X = \{x_1, x_2, x_3\}, \quad Y = \{y_1, y_2\}, \quad S = \{s_1, s_2, s_3, s_4\}, \quad s_I = s_1$$

$\delta / \lambda$	$x_1$	$x_2$	$x_3$
$s_I = s_1$	$s_2 / y_1$	$s_3 / y_2$	$s_2 / y_1$
$s_2$	$s_1 / y_2$	$s_3 / y_2$	$s_2 / y_1$
$s_3$	$s_3 / y_1$	$s_2 / y_1$	$s_4 / y_1$
$s_4$	$s_3 / y_2$	$s_1 / y_2$	$s_4 / y_2$

 

# Mealy Automata

Definition: An automaton is **deterministic**, if :

$$\forall x \in X, \forall s \in S : | \delta(s, x) | \leq 1$$

Definition: An automaton is **complete**, if:

$$\forall x \in X, \forall s \in S : | \delta(s, x) | \geq 1$$


→ The following is always true for deterministic complete automata:

$$\forall x \in X: \forall s \in S : | \delta(s, x) | = 1$$

- We limit ourselves in this class to deterministic and complete automata
  - Non-complete automata **model incomplete specifications**
  - Non-deterministic automata are used in **analysis and verification of sequential circuits**

 
# Mealy Automata Example 1

- Design a mealy machine that scans sequence of input of 0 and 1 and generates output 'A' if the input string terminates in 00, output 'B' if the string terminates in 11, and output 'C' otherwise.



 
# Mealy Automata Example 2

- Design a Mealy machine for a binary input sequence such that if it has a substring 101, the machine output A, if the input has substring 110, it outputs B otherwise it outputs C.



# Mealy Automata – Finite State Machines

 

- Finite State Machine = Technical realization of automata
- The structure is known as Huffman Normal Form
- Symbols ( $X, Y, S$ ) used for modeling must first be binary coded for a logic implementation:
  - $x_1 \dots x_n$  binary input variables
  - $y_1 \dots y_m$  binary output variables
  - $s_1 \dots s_p$  binary state variables
  - $s_1^+ \dots s_p^+$  next state

# Design of Sequential Circuits

- The design of synchronous sequential circuits is done in the following steps:
  1. Specify the automaton using state transition table/graph
    - If needed, minimize the number of states (more on this later)
  2. Compute binary coding of the inputs and outputs  
Compute the number of **memory cells** needed to store the states
  3. Specify the combinational circuits for the functions  $\delta$  and  $\lambda$  resp.
    - $\mu$  from the state transition table:  $S^+ = \delta(X, S)$  and  $Y = \lambda(X, S)$  resp.  $Y = \mu(S)$
  4. Design of the combination functions as 2-level or multi-level logic
  
- The minimization of gates and flip flops is a complex problem
  - In the next, we will learn
    - Automata equivalency and state minimization
    - Coding

# Case Study

- A "mean" vending machine
  - The machine expects in its initial state a \$1
  - The user can then choose between
    - Coke and
    - 7up, or
    - press the R-button to get his money back
  - If the user inserts \$2 (1 additional \$) the automat returns to its initial state



# A "mean" Vending Machine

- Specification with automata: input , output

Inputs:  $X = \{\$, C, 7, R\}$

- \$ ... Money (\$1) inserted
- C ... Coke selected
- 7 ... 7up selected
- R ... „Refund“ selected

Outputs  $Y = \{GC, G7, M, \emptyset\}$

- GC ... Give Coke
- G7 ... Give 7up
- M ... Return 1\$
- $\emptyset$  ... Do nothing

# A "mean" Vending Machine

- Specification as Mealy automaton: states, state transition table

States  $S = \{I, H\}$

- $I$  ... Initial state
- $H$  ... Automaton has \$1

State transition table

- Specifies  $\delta$  and  $\lambda$
- Initial state  $s_I = I$

$\delta / \lambda$	\$	C	7	R
$I$	$H / \emptyset$	$I / \emptyset$	$I / \emptyset$	$I / \emptyset$
$H$	$I / \emptyset$	$I / GC$	$I / G7$	$I / M$

# A "mean" Vending Machine

- **Binary coding** of inputs, outputs and states
  - 4 input symbols can be represented **with 2 bits**  $(x_1, x_0)$  code, for example
$$X = \{\$, C, 7, R\} \rightarrow (x_1, x_0) = \{00, 01, 10, 11\}$$
  - 4 input symbols can be represented **with 2 bits**  $(y_1, y_0)$  code, for example
$$Y = \{GC, G7, M, \emptyset\} \rightarrow (y_1, y_0) = \{00, 01, 10, 11\}$$
  - 2 states can be represented **with just 1 Bit**  $(s)$ 
$$S = \{I, H\} \rightarrow (s) = \{0, 1\}$$


# A "mean" Vending Machine

- Specification of  $\delta$  and  $\lambda$  using state transition table
  - Devise truth table of  $S^+ = \delta(X, S)$  and  $Y = \lambda(X, S)$  from state transition table

$\delta/\lambda$	$S$	$C$	$7$	$R$
$I$	$H/\emptyset$	$I/\emptyset$	$I/\emptyset$	$I/\emptyset$
$H$	$I/\emptyset$	$I/GC$	$I/G7$	$I/M$

State transition table with binary codes

$\delta/\lambda$	00	01	10	11
0	1 / 11	0 / 11	0 / 11	0 / 11
1	0 / 11	0 / 00	0 / 01	0 / 10

 

Truth table

$s$	$x_1$	$x_0$	$s^+$	$y_1$	$y_0$
0	0	0	1	1	1
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	1	0

# A "mean" Vending Machine

- Compute the combinational functions for  $\delta$  and  $\lambda$

$s$	$x_1$	$x_0$	$s^+$	$y_1$	$y_0$
0	0	0	1	1	1
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	1	0

$$s^+ = \bar{s} \bar{x}_1 \bar{x}_0$$

$$y_1 = \bar{s} + x_1 x_0 + \bar{x}_1 \bar{x}_0$$

$$y_0 = \bar{s} + \bar{x}_0$$

$x_1$				$s$
0	0	0	0	
0	0	0	1	

$x_0$

$x_1$				$s$
0	1	0	1	
1	1	1	1	


$x_0$

$x_1$				$s$
1	0	0	1	
1	1	1	1	

$x_0$

# A „mean" Vending Machine

- FSM

 

```



LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY FSA_MEALY IS

PORT( clk, reset: IN std_logic;
      x,yz: IN std_logic;
      a,c: OUT std_logic);
END FSA_MEALY F;

ARCHITECTURE specific OF FSA_MEALY
TYPE state_type IS (Q0, Q1, Q2, Q3) ;
SIGNAL current_state, next_state: state_type ;

```

  

Transitions

Outputs in transitions

```

Comb : PROCESS ( current_state )
BEGIN
CASE current_state IS
WHEN Q0 =>
IF ( z = '1' ) THEN
next_state <= Q1 ; a <= ,1';
END IF
IF ( x = '1' or y = '1' ) THEN
next_state <= Q3 ; c <= ,1';
END IF

WHEN Q1 =>
IF ( y = '1' ) THEN
next_state <= Q2 ; a <= ,1';
END IF
IF ( x = '1' or y = '1' ) THEN
next_state <= Q3 ; c <= ,1';
END IF

...
END CASE;
END PROCESS Comb;

```

```

...
Synch : PROCESS ( CLK, RESET )
BEGIN

IF ( RESET = '1' ) THEN -- asynchronous reset
CURRENT_STATE <= Q0;
ELSIF ( CLK'EVENT and CLK = '1' ) THEN
CURRENT_STATE <= NEXT_STATE;
END IF;

END PROCESS Synch;

```

# Moore Automata

Definition: A **Moore automaton** is a tuple  $A=(X, Y, S, \delta, \mu, s_I)$  where

$X$ : finite , non-empty set of **input symbols**

$Y$ : finite, non-empty set of **output symbols**

$S$ : finite, non-empty set of **state symbols**

$\delta: S \times X \rightarrow S$       **state transition function**

$\mu: S \rightarrow Y$             **output function**


$s_I$ :                        **initial state**

- **Difference between Mealy and Moore automata**
  - Moore Automata: The output  $Y$  depends only on the current state, **not the input**
  - The output function is also known as **state marking function**


# Moore – State Transition Table/Graph

$$X = \{x_1, x_2, x_3\}, \quad Y = \{y_1, y_2\}, \quad S = \{s_1, s_2, s_3, s_4\}, \quad s_I = s_1$$

	<u><math>\mu</math></u>	<u><math>\delta</math></u>		
		$x_1$	$x_2$	$x_3$
$s_I = s_1$	$y_1$	$s_2$	$s_3$	$s_2$
$s_2$	$y_2$	$s_1$	$s_3$	$s_2$
$s_3$	$y_2$	$s_3$	$s_2$	$s_4$
$s_4$	$y_1$	$s_3$	$s_1$	$s_4$

 


# Moore Automata - Structure

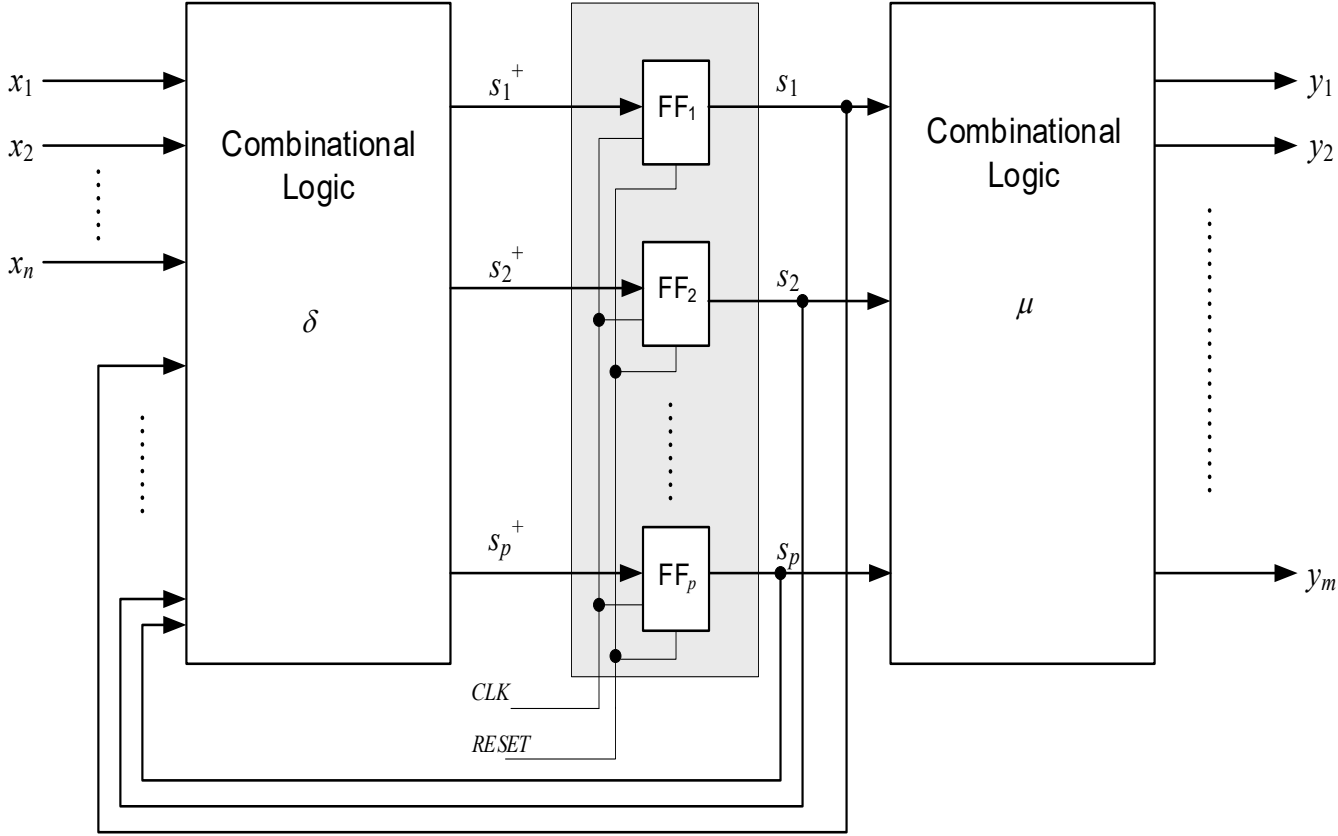
 
# Moore Automata Example

- Design a Moore machine for a binary input sequence such that if it has a substring 101, the machine output A, if the input has substring 110, it outputs B otherwise it outputs C.



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY FSA_MEALY IS
```

```
PORT( clk, reset: IN std_logic;
      x,y,z: IN std_logic;
      a,c: OUT std_logic);
```

```
END FSA_MEALY F;
```

```
ARCHITECTURE specific OF FSA_MEALY
TYPE state_type IS (Q0, Q1, Q2, Q3);
SIGNAL current_state, next_state: state_type;
```

```
Comb : PROCESS ( current_state )
```

```
BEGIN
```

```
  CASE current_state IS
```

```
    WHEN Q0 =>
```

```
      a <= '1';
```

```
      IF ( z = '1' ) THEN
```

```
        next_state <= Q1 ;
```

```
      END IF
```

```
      IF ( x = '1' or y = '1' ) THEN
```

```
        next_state <= Q3 ;
```

```
      END IF
```

```
    WHEN Q1 =>
```

```
      a <= '1';
```

```
      IF ( y = '1' ) THEN
```

```
        next_state <= Q2 ;
```

```
      END IF
```

```
      IF ( x = '1' or z = '1' ) THEN
```



```
        next_state <= Q3 ;
```

```
      END IF
```

```
    ...
```

Outputs in the states independent of transitions

Transitions

 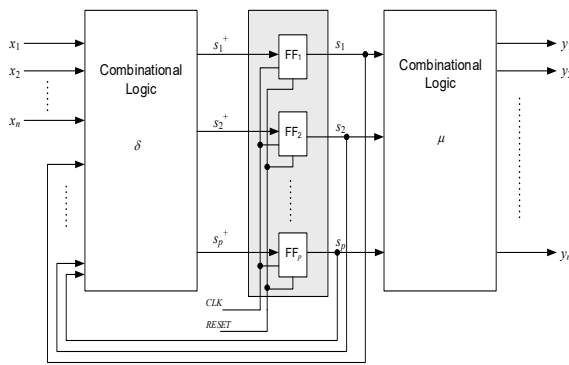

```
...
```

```
Synch : PROCESS ( CLK, RESET )
```

```
BEGIN
```

```
  IF ( RESET = '1' ) THEN -- asynchronous reset
```

```
    CURRENT_STATE <= S0;
```

```
  ELSIF ( CLK'EVENT and CLK = '1' ) THEN
```


```
    CURRENT_STATE <= NEXT_STATE;
```

```
  END IF;
```

```
END PROCESS Synch;
```
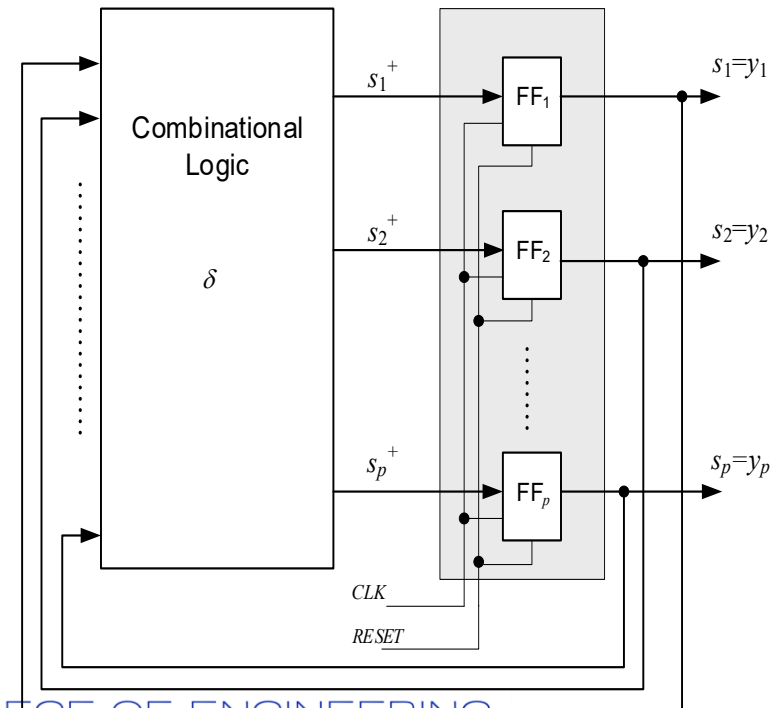
# Case Study: Synchronous Counter


- Synchronous counters can be built using Moore automata
  - No input, i.e.  $X = \{ \}$
  - No output function  $\mu$ , i.e. the binary codes of the states are the identical to the outputs



# Conversion - Moore to Mealy


- A Moore-automaton is converted in an equivalent Mealy-automaton, by **marking transitions with the output symbol of the target state**

- Example

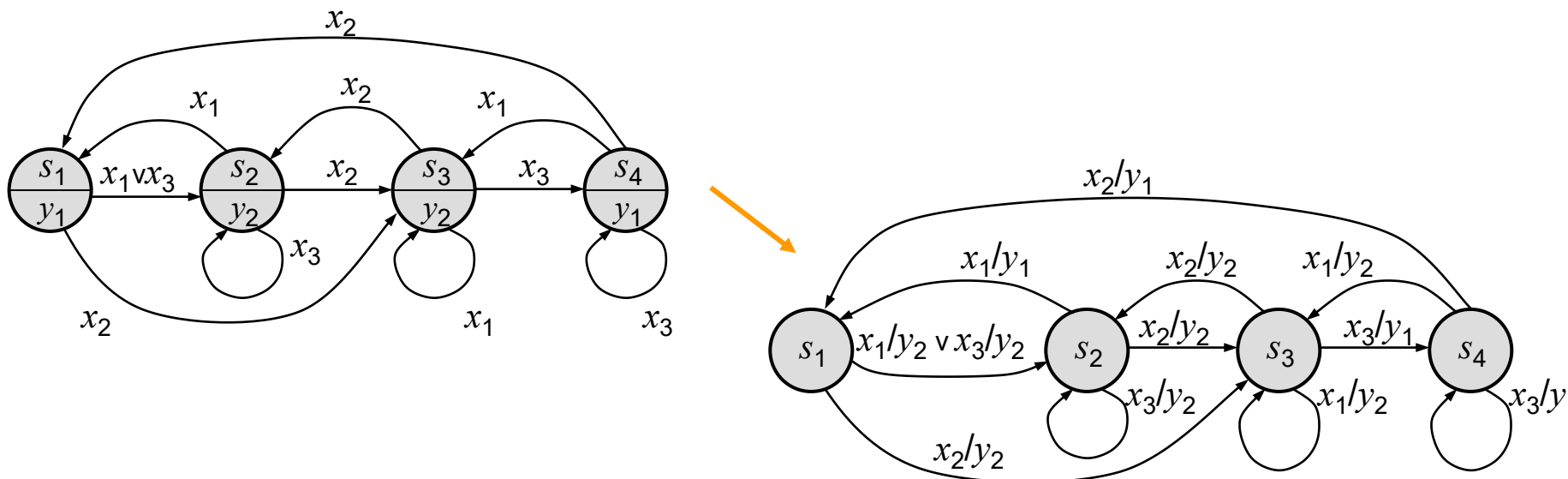

 
# Conversion - Mealy to Moore

- For each state  $s$  of the Mealy automaton, insert as many states as there are incident edges to  $s$ . Label the new states with the output variables of the corresponding incident transitions






- Resulting automaton can be reduced

- Example

 
   
# Exam Statistics

- p-values: lab =  $2.39e-08$ , attendance =  $1.28e-05$ . Smaller values mean more statistical significance, 0.05 is a good benchmark and we're way below that.
- Every +3 points to overall lab score = +1 exam point, every +7 attendance points = +1 exam point.
- Mean: 83.4, Median: 87.0, 25th percentile: 78.25, 75th percentile: 94.0.
- 43.9% got a 90 or higher, 71.4% got an 80 or higher, 86.9% got a 70 or higher.
- TLDR: Go to class and focus on labs and you do better on exams.





# iClicker Question

What is the difference between Mealy and Moore?

- A) Mealy machines are more robust for short impulses of the inputs
- B) Moore machines are more robust for short impulses of the inputs
- C) Moore machines react faster to changes at the input
- D) Mealy machines react faster to changes at the input

  
# Conversion - Moore to Mealy

- Convert the following Moore automaton into a Mealy automaton



 
# Conversion - Moore to Mealy

- Convert the following Moore automaton into a Mealy automaton



 
# Conversion - Moore to Mealy

- Convert the following Mealy automaton into a Moore automaton



 
# Conversion - Moore to Mealy

- Convert the following Mealy automaton into a Moore automaton



 
# Conversion - Moore to Mealy

- Convert the following Mealy automaton into a Moore automaton


 
# Conversion - Moore to Mealy

- Convert the following Mealy automaton into a Moore automaton





**UF** | Herbert Wertheim  
College of Engineering  
UNIVERSITY *of* FLORIDA

---

LEADING THE CHARGE, CHARGING AHEAD