 


VHDL-Overview

Christophe Bobda

VHDL



VHDL: **V**ery high speed integrated circuits **H**ardware

~~Very Hard Design Language~~

Hardware-Description Language with the goals

Simulation

IC synthesis



Description is done under the aspects

Behavior

Structure

Hierarchy

Parallelism

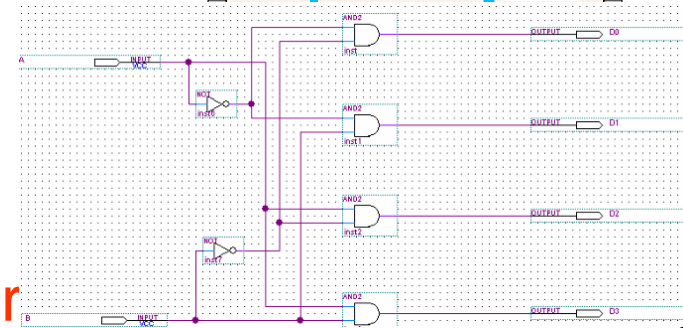
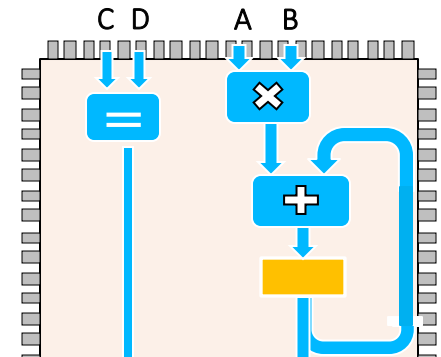


Only synthesizable Subset is consider

a	b	c	f	h
0	0	0	0	1
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

$$f = \bar{a}\bar{b}\bar{c} + a\bar{b}c + abc$$
  
$$h = \bar{a}\bar{b}\bar{c} + a\bar{b}\bar{c} + abc$$




a	b	f	g	h
0	0	1	0	1
0	1	0	0	1
1	0	1	1	0
1	1	0	1	1

$$f = \bar{a}\bar{b} + a\bar{b}$$

$$g = a\bar{b} + ab$$

$$h = \bar{a}\bar{b} + \bar{a}b + ab$$

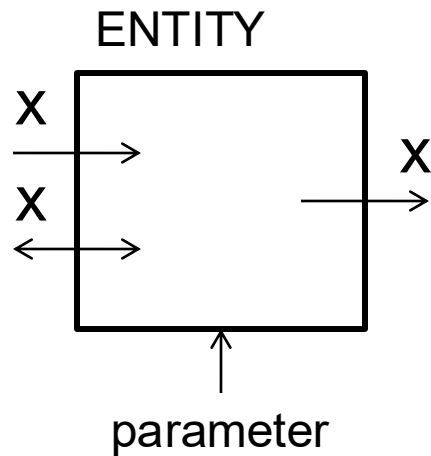Entity – Wrapper and interface definition




logic encapsulation of a unit Interface

Definition: **Port** \rightarrow X


Port are defined through **Identifier**,
Direction und **Data-type**

Direction: **in**, **out**, **inout**, **buffer**

Data-type: bit, std_logic(_vector), ADT

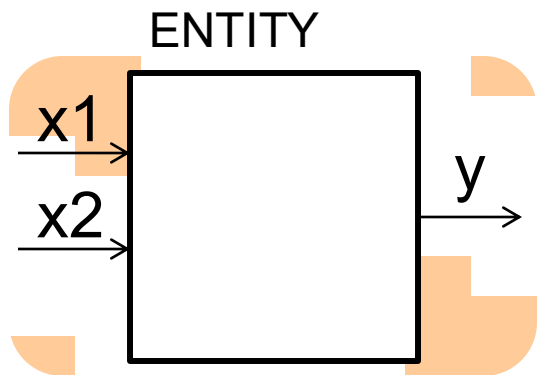

View from outside

 

View from inside

Signals can be connected to ports from inside or from outside.


Entity as „Black Box“

Viewed from outside an entity is a „black box“

→ The structure and behavior (functionality) is hidden

Example below: Entity with two inputs and one output port

Functionality not defined yet

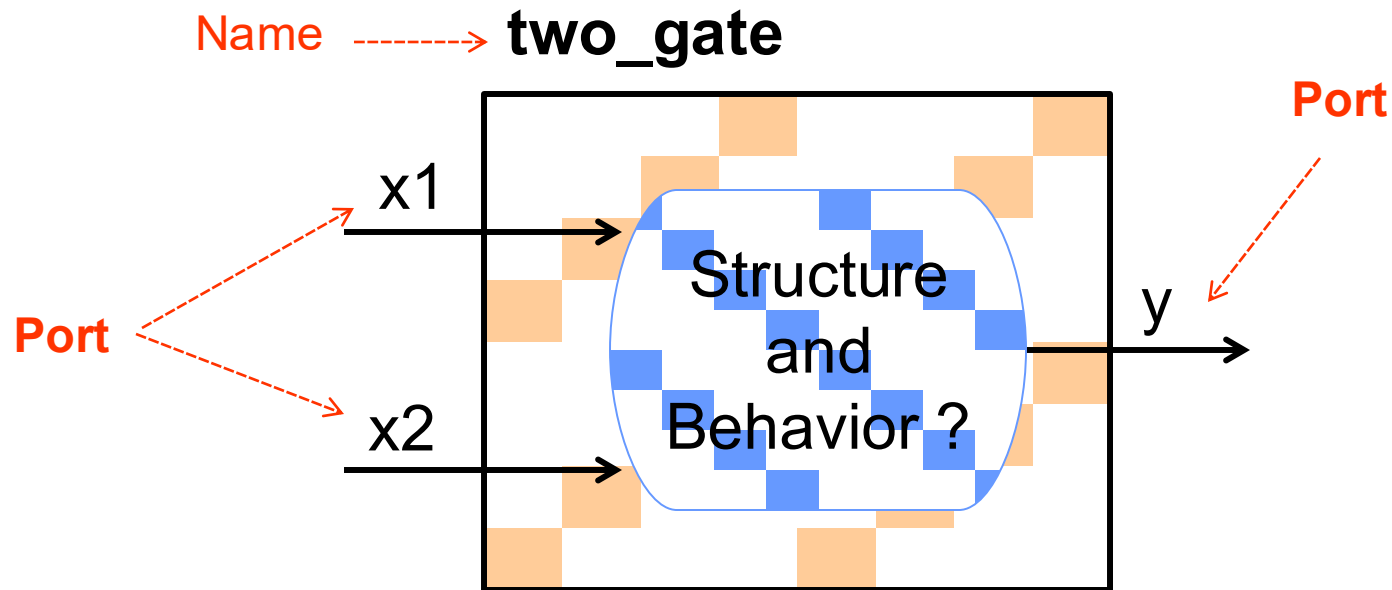

Entity – Definition

Keywords in blue

Library to be used

Which part of the library should be

Prefix

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

Entity-Definition

```
ENTITY two_gate IS
```

Interface

```
PORT (x1, x2 : IN std_logic;
      y      : OUT std_logic);
```

```
END two_gate;
```

Name of the Entity

Output-Signal with name: y

Data-type of the signal
(multi-value logic)


VHDL is case insensitive !

Architecture – Behavior of the Entity

The behavior of an Entity is described in the **Architecture**.

The Architecture

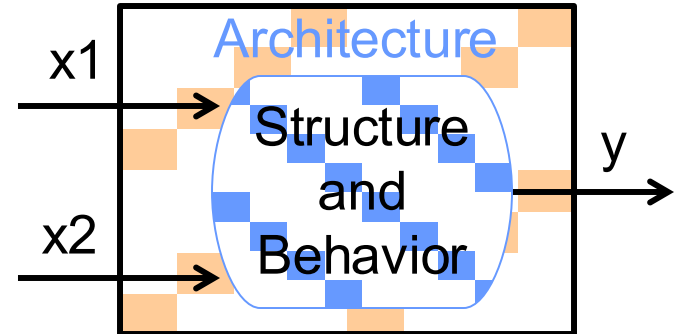- has a unique name,
- signals and components can be internally declared,
- is assigned to a unique Entity.




```
ARCHITECTURE <Architecture name> OF <Entity-Name> IS  
[Declarations]  
BEGIN  
    [Architecture Statements]  
END <Architecture name>;
```

Architecture – Example

NAND-Gate

based on the previous Entity-Definition:

 

Signal assignment

Architecture name

Entity name

```
ARCHITECTURE two_gate_nand OF two_gate IS  
BEGIN
```

```
y <= NOT ( x1 AND x2 );
```

```
END two_gate_nand;
```

Behavioral description:

one statement with pre-defined and pre-implemented functions: AND, OR, NOT

Architecture name

XOR-Entity

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY xor_gate IS

PORT( x1, x2  : IN    std_logic;
      y       : OUT  std_logic );
END xor_gate;

ARCHITECTURE behavioral OF xor_gate IS
BEGIN

    y <= x1 XOR x2;

END behavioral;
```

VHDL Operators

Signal Assignment: $y \leq x1$

Boolean Operators:

- **AND/and:** logical and
- **OR/or:** logical or
- **NAND/nand:** logical complement of and
- **NOR/nor:** logical complement
- **XOR/xor:** logical exclusive
- **XNOR/xnor:** logical complement of exclusive

**Random Boolean statement can be specified in VHDL.
Use parentheses to enforce precedence**

$y \leq (x1 \text{ XOR } \text{NOT}(x2 \text{ XOR } X3)) \text{ NAND } y;$

Process – Parallel statements

VHDL describes parallel processes

- All signal assignments take place simultaneously

<u>VHDL</u>		<u>VHDL</u>
A <= B;	=	C <= D;
C <= D;		A <= B;

<u>VHDL</u>		<u>JAVA</u>
A <= B;	≠	A = B;
C <= A;		C = A;

Example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY my_circuit IS

PORT( a, b      : IN      std_logic;
      x, y, z   : OUT    std_logic );
END my_circuit ;

ARCHITECTURE behavioral OF my_circuit IS
BEGIN
    y <= a XOR (a AND NOT(b));
    z <= b OR NOT b;
    x <= b OR NOT b;
END behavioral;
```

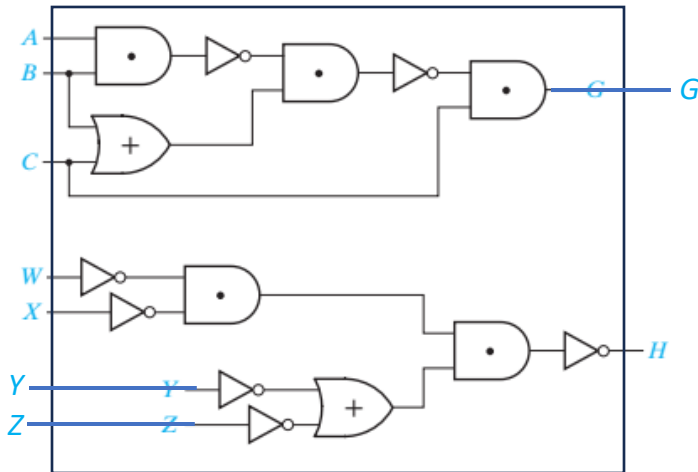Example

Provide the VHDL design for the circuit below



```
ENTITY example2 IS
PORT( A : IN          std_logic;
      w,y, b,c : IN   std_logic;
      z,x      : IN   std_logic;
      H       : OUT   std_logic;
      g       : OUT   std_logic );
END entity example2;
```

Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY example2 IS
PORT( A, B, c : IN          std_logic;
      w,y      : IN        std_logic;
      z       : IN        std_logic;
      x       : IN        std_logic;
      H, g    : OUT        std_logic );
END example2;
```

Architecture Implementation


```
architecture structural arc IS
begin

g <= c AND NOT((b OR c) AND (NOT(a AND b)));
H <= NOT(NOT Y OR NOT z) AND (NOT W AND NOT X);

END architecture;
```

iClicker Question

 Given the following circuit diagram, choose the correct implementation in VHDL:



```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity iClicker is  
port ( a : in std_logic;  
       b : in std_logic;  
       c : in std_logic;  
       d : out std_logic  
);  
end iClicker;
```

```
architecture structural is  
begin
```

- A** $d \leq a \text{ and } b \text{ nor } c$
- B** $d \leq (a \text{ and } c) \text{ or } (b \text{ and } c)$
- C** $d \leq ((a \text{ and } b) \text{ or } c) \text{ and } b$
- D** $d \leq a \text{ and } b$

```
end architecture;
```

Design Flow

Modern design is done using CAD (computer-aided design) or EDA (Electronic Design Automation) tools

- FPGA: AMD Vivado, ~~Intel~~ Altera Quartus
- VLSI: Synopsys DC, Cadence,

Design Flow: See Lab0

- Design Entry
- Functional Simulation
- Synthesis (Pins and Library assignment, compilation)
- Post-synthesis simulation (timing analysis, verification)
- Place and Route (Layout)
- Fabrication/Bitstream Download (FPGA)

Signals

- A signal defines a **connection in hardware**. Can be used to connect components within an entity
- A signal has a **datatype**, which is the of possible values + operations on those values
- Signal Declaration

SIGNAL *signal_name1* [, *signal_name2*, ...] : *signal_type* ;

- Declaration can be done in
 - Package
 - Port-section of an entity
 - Declaration section of an entity
- Signal Assignment is performed with symbol `<=`
a <= b xor c

Internal Signals

ENTITY Position IS

PORT(A : in std_logic_vector(2 downto 0);

B : out std_logic_vector(0 to 2));

END Position;

ARCHITECTURE behv OF Position IS

SIGNAL signal1, signal2: std_logic;

SIGNAL signal3 : std_logic_vector(4 downto 0);

Begin


signal1 <= A(0) AND B(2);

B(0) <= signal1 XOR A(1);

...

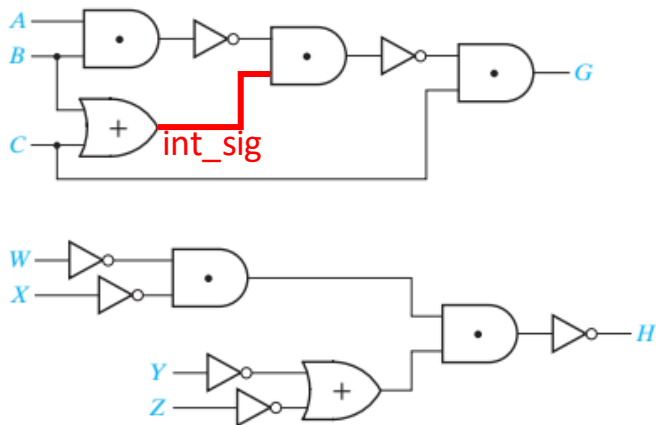
Example

Provide the VHDL design for the circuit below



Signals not connected are floating and will be removed by the compiler

 Assigning multiple values to a signal simultaneously will create a multi-drive situation.



Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY example2 IS
PORT( A, B, c : IN      std_logic;
      w,y  : IN      std_logic;
      z    : IN      std_logic;
      x    : IN      std_logic;
      H, g : OUT     std_logic );
END example2;
```

Architecture Implementation

```
architecture structural arc IS
  signal int_sig: std_logic;
begin
  int_sig <= (b OR c);
  g <= c AND (int_sig AND (NOT(a AND b)));
  H <= NOT(NOT Y OR NOT z) AND (NOT W AND NOT X);
END architecture;
```

Write(assign a value) to the signal

Read from the signal

Variables

- A variable defines a **memory location**. Can be used to store values.
- A variable has a **datatype**, which is the set of all possible values + operations on those values
- Variable Declaration

VARIABLE *var_name1*[, *var_name2*, ...] : *variable_type*;

- Declaration can be done **exclusively in a process**
- Variable assignment is performed with symbol **:=**
a := b xor c

```
PROCESS(a, b)
  VARIABLE c: bit;

  c := b and c;
```

Datatypes

Datatype

- Define a **set of values** a signal or a variable can take, along with operations on those values.
- Predefined datatype
 - bit (std_logic): '0', '1'
 - bit_vector (std_logic_vector): "00101", "001001"
 - integer: 10, 123, 56
 - character: 'a', 'v', 'n'
 - string: "anmggzem"
 - Boolean: FALSE, TRUE
 - real: 1.23, 234.6, -0.34
- User-defined datatype
 - SATES
 - CAN_PARAMETERS
 - NETWORK_PACKET
 - ...

Multi-Value Logic


- Standard logic IEEE 1164
 - Std_logic instead of bit
 - Declaration in Package „standard_logic_1164“
 - Possible values:
 - ‘U’ not initialized
 - ‘X’ unknown
 - ‘0’ Logic 0
 - ‘1’ Logic 1
 - ‘Z’ high impedance
 - ‘W’ unknown (weak signal)
 - ‘L’ logic 0 (weak signal)
 - ‘H’ Logic 1 (weak signal)
 - ‘-’ Don't care
 - Standard_logic_vector: Vektor von standard_logic values

Bit vectors

Single signals can be grouped in a vector:

`std_logic` → `std_logic_vector()`

Example: 3-bit coded position

 


ENTITY Position IS

PORT(A : in std_logic_vector(**2 downto 0**);

B : out std_logic_vector(0 to 2));

END Position;

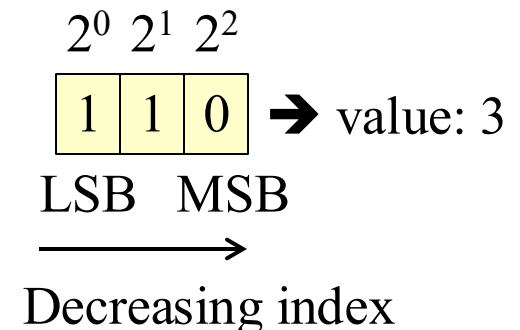3-bit wide, binary coded Bit-vector,
write: x **downto** y means decreasing index from
the MSB to the LSB
(MSB: most significant bit, LSB: least ...)




Bit (Std_Logic) Vectors

- Declaration
 - `signal Z_Bus: bit_vector(3 downto 0);`
 - `signal Z_Bus: std_logic_vector(0 to 3);`
- Assignment:
 - “By position”
 - `Z_Bus(3) <= C_Bus(1);`
 - `Z_Bus(1) <= C_Bus(1);`
 - `Z_Bus(3 downto 2) <= “01”`
 - “Concatenation”:
 - `Z_Bus <= A & B & C & D;`
 - “Aggregates”:
 - `Z_Bus <= (A, B, C, D);`
 - “Specifying by element index”:
 - `Z_Bus <= (3 => ‘ 1’, 1 downto 0 => ‘ 1’, 2 => ‘ 0’);`
 - “others”:
 - `Z_Bus <= (3 => ‘ 1’, 1 => ‘ 0’, other => ‘ 0’);`

VHDL Operators

- Logic operators
 - **AND, OR, NAND, NOR, XOR** (equal precedence)
 - **NOT** (higher precedence)
- comparison
 - **<** (smaller than), **<=** (smaller or equal than), **=** (equal), **>=** (bigger or equal) , **>** (bigger than), **/=** (different)
- Arithmetic operators
 - **+** (Addition), **-** (subtraction), ***** (Multiplication), **/** (Division), ****** (Exponent), **abs** (Magnitude), **mod** (Modulo), **rem** (Remainder)

Want To Learn More ?

 

Consider Undergraduate
Research With Us/Other Labs

<https://smartsystems.ece.ufl.edu/>

