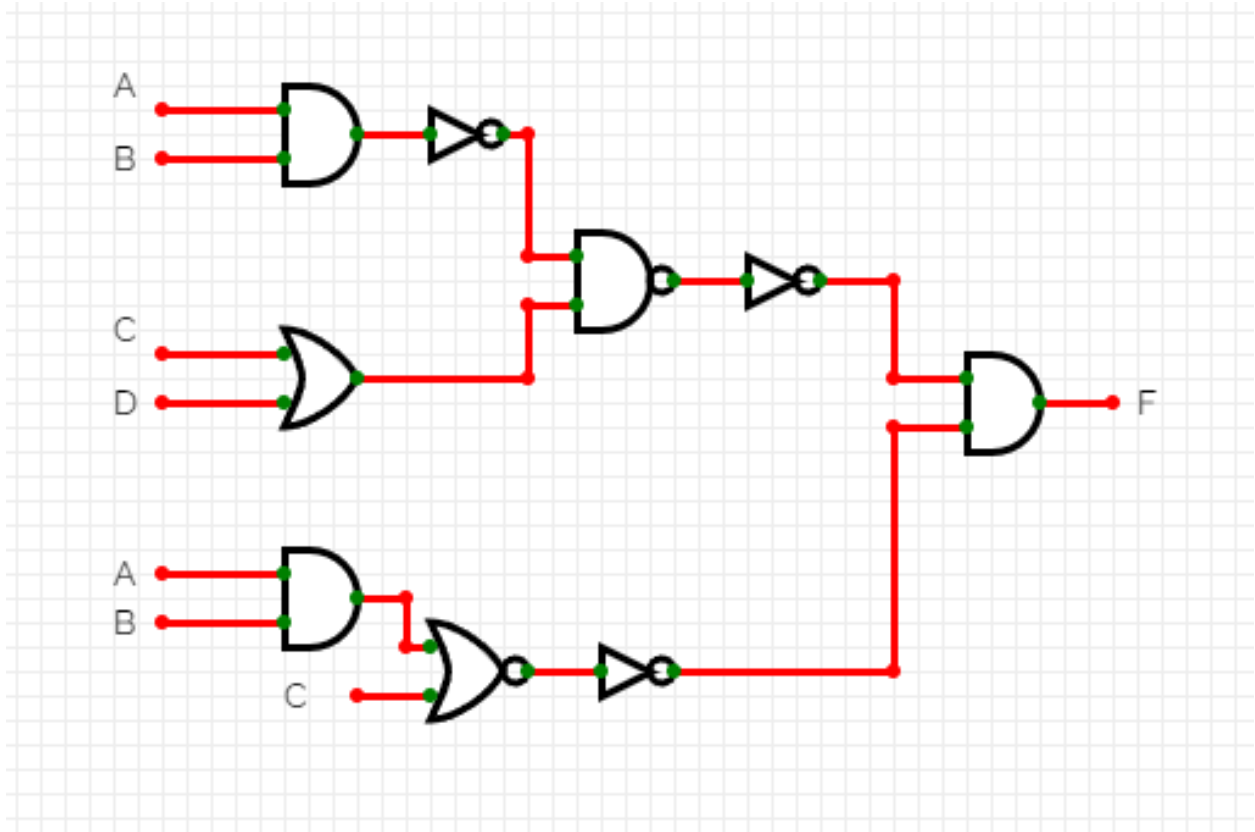


1. Design a combinational circuit diagram that takes in 3 inputs and produces 1 output. The output should be true whenever exactly 2 of the 3 inputs are true.

- A. Define the 3 inputs and the 1 output for your circuit.
- B. Create a truth table for the circuit
- C. Draw the circuit design.

2. Provide the value of the logic function F. Provide an unsimplified version, then a simplified version using K-Maps or Boolean Algebra rules.



3. Derive the MPOS and MSOP equations for this k-map.

		CD			
AB		00	01	11	10
00	1	0	1	1	
01	1	0	1	1	
11	1	1	0	0	
10	1	1	1	1	

4. Derive the equations for a 2x1 multiplexer. Then create a 4x1 multiplexer out of 2x1 multiplexers. Finally, create a 8x1 multiplexer with 4x1 and 2x1 multiplexers.

5a. Explain the behavior of an encoder. What are its inputs and outputs?

5b. Explain the behavior of a decoder. What are its inputs and outputs?

6a. What is an SR latch?

6b. What is a flip-flop?

6c. What is the purpose of the clock signal?

6d. What is the difference between an asynchronous and synchronous component?

7. Create a 3-bit counter that counts in the sequence 4 → 7 → 1 → 2 → C → 4 → 7 → ... using only D-FFs. There should be an asynchronous reset that resets the counter to 4. (Remember: The state of a counter can be separate from its output).

You must:

- Create an NSTT with the state bits and flip-flop inputs
- Derive the equation for the flip-flop inputs using k-maps
- Create a circuit diagram with flip-flops and any necessary logic gates